

Report

Sketch the circuit diagram, explain the function of each component, and find the output signal of the following modulators:

1. Square-law modulator for DSBTC modulation
2. Ring modulator for DSBSC modulation

Submission deadline: 13/5/2012